

City College of New York

# Take Home Test # 1

Zi Xuan Li

CSC 211 Fall 2022

Professor Izidor Gertner

November 6<sup>th</sup>, 2022

## ***Objective:***

The objective of this report is to build, simulate, and verify the correctness of both Positive and Negative D-Latches that are built using 2:1 Multiplexers. This report will simulate D-Latches made using the template of a 2:1 Multiplexer symbol as well as 2:1 Multiplexer made using AND, OR, and NOT gates. Alongside that, the report will also include VHDL code for a Positive D-Latch as well as Negative D-Latch.

## ***Functionality, Specifications, and Simulation:***

To verify the correctness of these circuits we must understand how a Positive D-Latch as well as a Negative D-Latch works.

A Positive D-Latch works the exact same as a typical D-Latch. The functionality of the D-Latch is meant to capture or “latch” the logic which is present on the data signal when the CLK signal is high. That means, if the data on the D signal changes state (from 1 to 0 or from 0 to 1) while the CLK signal is high, then the output, Q, follows the input, D. When the CLK signal is low, the last state of the D signal is trapped and held in the latch and the output Q retains the previous value of D (the value before the CLK drops to 0).

A Negative D-Latch works similarly to the Positive D-Latch except that the output Q follows the input D when the CLK signal is low instead of high. That means, if the data on the D signal changes state while the CLK is low, then the output, Q, follows the input, D. When the CLK signal is high, the output Q retains the previous value of D (the value before the CLK rises to 1).

Using this information, we can form a truth table of a Positive D-Latch as well as a Negative D-Latch.

Positive D Latch		
CLK	D	Q(t)
0	0	Q (t – 1)
0	1	Q (t – 1)
1	0	0
1	1	1

Negative D Latch		
CLK	D	Q(t)
0	0	0
0	1	1
1	0	Q (t – 1)
1	1	Q (t – 1)

**Part 1: (Design and build in Quartus Positive D-Latch using 2:1 MUX using gates from the first lab)**

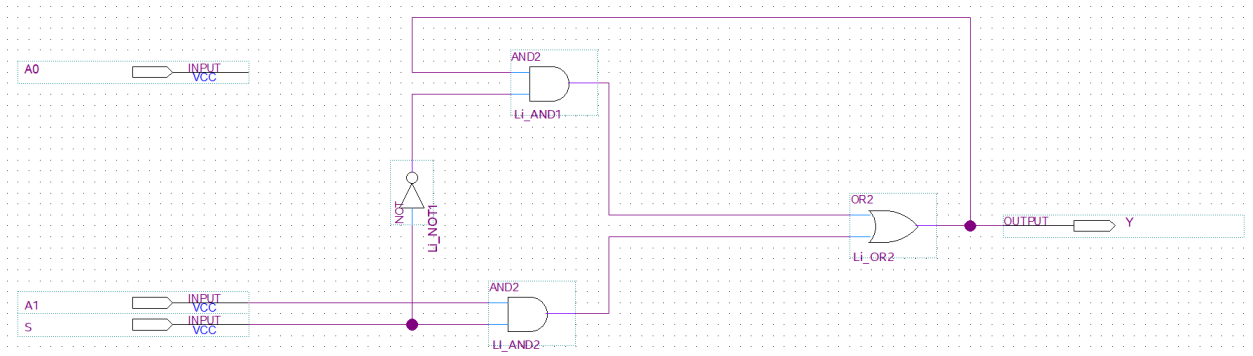


Figure 1: Positive D-Latch digital circuit built using the 2:1 Mux as a template with gates that we used in the first lab.

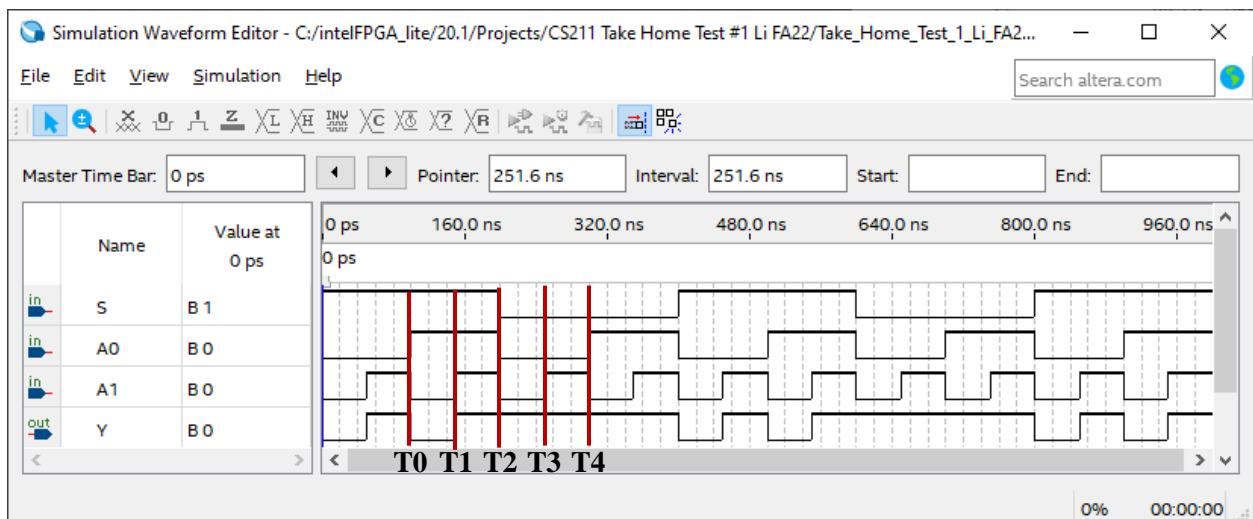


Figure 2: University Program VWF output for the D-Latch in figure 1 with input signals S, A0, A1 and output signals Y. In this waveform simulation, S represents standard input ENA/CLK with a period of 400ns and duty cycle of 50%. A0 is not used in the digital circuit. A1 represents standard input D with a period of 100 ns and duty cycle of 50%. Y represents the standard output Q of the D-Latch.

To verify the correctness of the digital circuit in Figure 1, I compared the VWF in Figure 2 with the truth table of a standard Positive D-Latch. In Figure 2, T0 to T1 shows that the output of the digital circuit when S (CLK) is HIGH and A1 (D) is LOW results in Y (Q) being LOW. T1 to T2 shows that the output when S is HIGH and A1 is HIGH results in Y being HIGH. T2 to T3 shows that the output when S is LOW and A1 is LOW results in Y being HIGH (latch case). T3 to T4 shows that the output when S is LOW and A1 is HIGH results in Y being HIGH (latch case). The results of the VWF matches all the possible cases of the Positive D-Latch truth table and thus it is correct.

The diagram illustrates a 2-bit majority gate circuit. It features two input registers, A0 and A1, each with two data inputs connected to VCC. A0's output is connected to the top input of AND2 and the top input of OR2. A1's output is connected to the bottom input of AND1 and the bottom input of OR2. A NOT gate (LI\_NOT1) is connected to A1's output, and its output is connected to the bottom input of AND2. The outputs of AND1 and AND2 are connected to the inputs of OR2. The output of OR2 is connected to the OUTPUT register, which is labeled Y.

Simulation Waveform Editor - C:/intelFPGA\_lite/20.1/Projects/CS211 Take Home Test #1 Li FA22/Take\_Home\_Test\_1\_Li\_FA22...

File Edit View Simulation Help

Search altera.com

Master Time Bar: 0 ps Pointer: 319.6 ns Interval: 319.6 ns Start: End:

	Name	Value at 0 ps
in	S	B 0
in	A0	B 0
in	A1	B 0
out	Y	B 0

0 ps 160.0 ns 320.0 ns 480.0 ns 640.0 ns 800.0 ns 960.0 ns

0 ps

T0 T1 T2 T3 T4

32% 00:00:30

To verify the correctness of the digital circuit in Figure 3, I compared the VWF in Figure 4 with the truth table of a standard Negative D-Latch. In Figure 4, T0 to T1 shows that the output of the digital circuit when S (CLK) is LOW and A1 (D) is LOW results in Y (Q) being LOW. T1 to T2 shows that the output when S is LOW and A1 is HIGH results in Y being HIGH. T2 to T3 shows that the output when S is HIGH and A1 is LOW results in Y being HIGH (latch case). T3 to T4 shows that the output when S is HIGH and A1 is HIGH results in Y being HIGH (latch case). The results of the VWF matches all the possible cases of the Negative D-Latch truth table and thus is correct.

**Part 3: (Design and build in Quartus Positive D-Latch using 2:1 MUX using Quartus component symbol)**

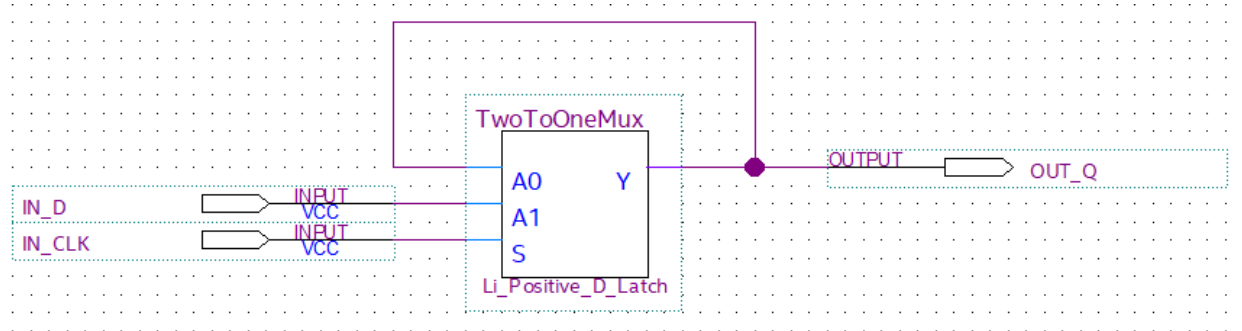


Figure 5: Positive D-Latch digital circuit built using the 2:1 Mux symbol as a component.

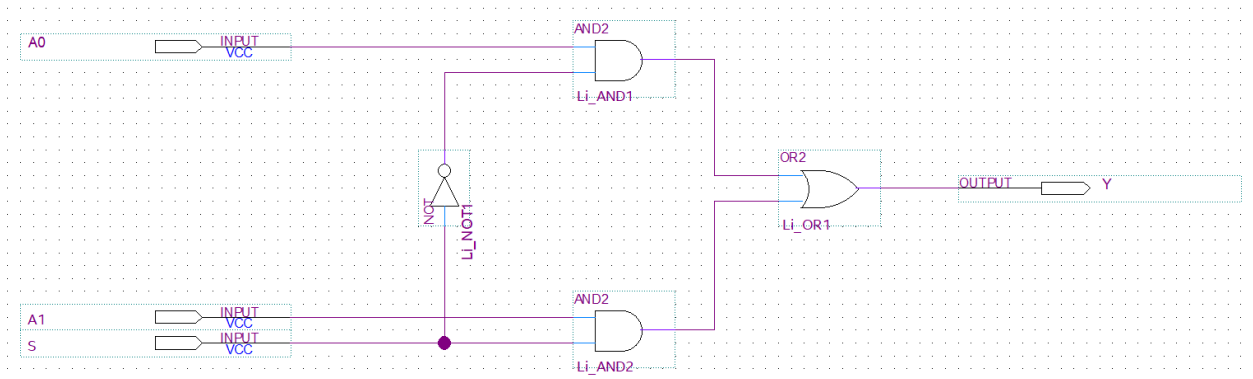


Figure 6: Digital Circuit of the 2:1 Mux Symbol being used in Figure 5.

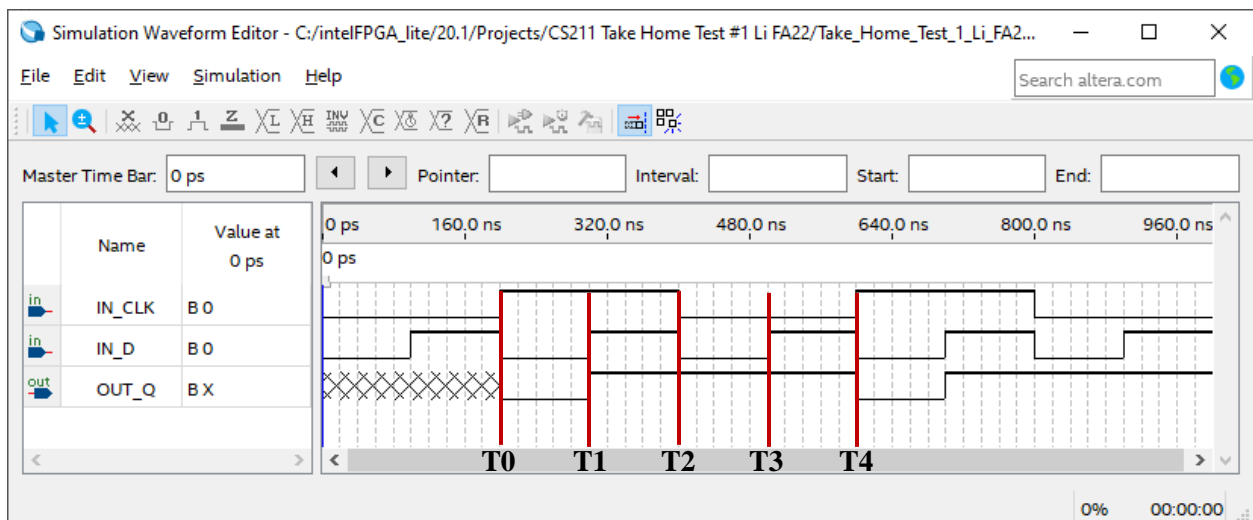


Figure 7: University Program VWF output for the D-Latch in figure 5 with input signals IN\_CLK and IN\_D and output signal OUT\_Q. In this waveform simulation, IN\_CLK has a period of 400ns and duty cycle of 50%. IN\_D has a period of 200ns and duty cycle of 50%. OUT\_Q represents the output.

To verify the correctness of the digital circuit in Figure 5, I compared the VWF in Figure 7 with the truth table of a standard Positive D-Latch. In Figure 7, T0 to T1 shows that the output of the digital circuit when IN\_CLK is HIGH and IN\_D is LOW results in OUT\_Q being LOW. T1 to T2 shows that the output when IN\_CLK is HIGH and IN\_D is HIGH results in OUT\_Q being HIGH. T2 to T3 shows that the output when IN\_CLK is LOW and IN\_D is LOW results in OUT\_Q being HIGH (latch case). T3 to T4 shows that the output when IN\_CLK is low and IN\_D is HIGH results in OUT\_Q being HIGH (latch case). The results of the VWF matches all the possible cases of the Positive D-Latch truth table and thus is correct.

#### Part 4: (Design and build in Quartus Negative D-Latch using 2:1 MUX using Quartus component symbol)

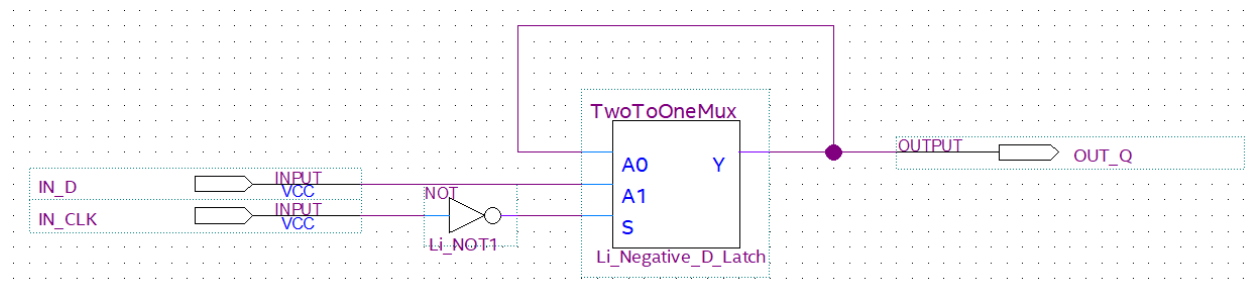


Figure 8: Negative D-Latch digital circuit built using the 2:1 Mux symbol as a component (2 to 1 Mux component is the same refer to figure 6).

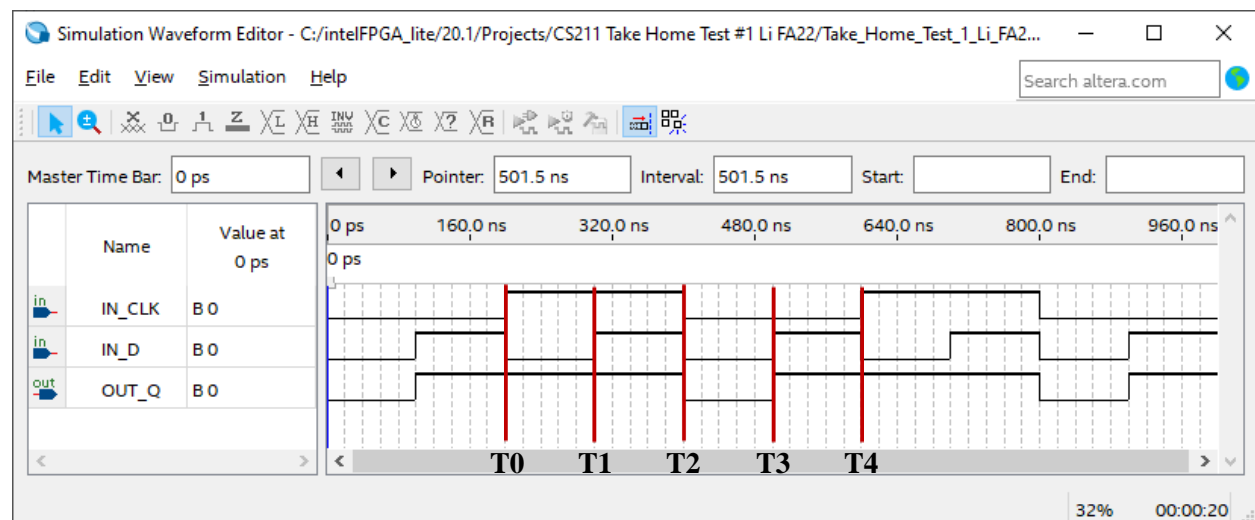


Figure 9: University Program VWF output for the D-Latch in figure 5 with input signals IN\_CLK and IN\_D and output signal OUT\_Q. In this waveform simulation, IN\_CLK has a period of 400ns and duty cycle of 50%. IN\_D has a period of 200ns and duty cycle of 50%. OUT\_Q represents the output.

To verify the correctness of the digital circuit in Figure 8, I compared the VWF in Figure 9 with the truth table of a standard Negative D-Latch. In Figure 9, T0 to T1 shows that the output of the digital

circuit when IN\_CLK is HIGH and IN\_D is LOW results in OUT\_Q being HIGH (latch case). T1 to T2 shows that the output when IN\_CLK is HIGH and IN\_D is HIGH results in OUT\_Q being HIGH (latch case). T2 to T3 shows that the output when IN\_CLK is LOW and IN\_D is LOW results in OUT\_Q being LOW. T3 to T4 shows that the output when IN\_CLK is low and IN\_D is HIGH results in OUT\_Q being HIGH. The results of the VWF matches all the possible cases of the Positive D-Latch truth table and thus is correct.

**Part 5: (Write VHDL code for Positive D-Latch, Negative D-Latch. Create a separate Quartus project for each)**

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Positive_D_Latch is
5  Port ( D : in  STD_LOGIC;
6        EN : in  STD_LOGIC;
7        Q : out STD_LOGIC);
8  end Positive_D_Latch;
9
10 architecture Behavioral of Positive_D_Latch is
11     signal DATA : STD_LOGIC;
12 begin
13
14     DATA <= D when (EN = '1') else DATA;
15     Q <= DATA;
16
17 end Behavioral;

```

Figure 10: Positive D-Latch VHDL Code.

 


Figure 11: BDF file of the VHDL code generated from Figure 10 into a symbol with inputs and outputs.

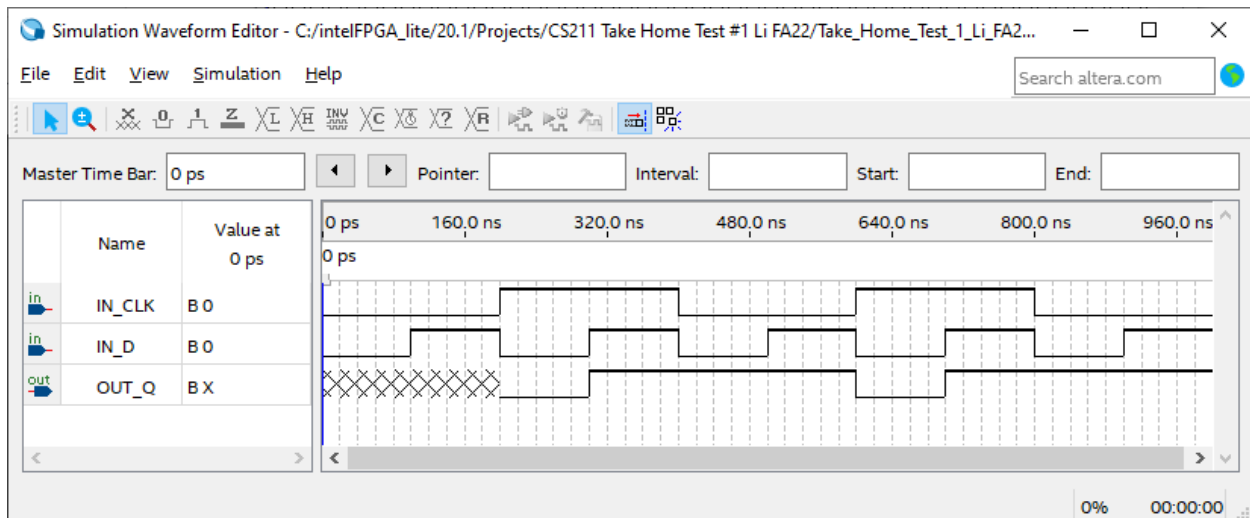


Figure 12: VWF output of the VHDL Code in Figure 10 generated as a symbol with input signals IN\_CLK and IN\_D and output signal OUT\_Q.

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Negative_D_Latch is
5  Port ( D : in  STD_LOGIC;
6        EN : in  STD_LOGIC;
7        Q : out STD_LOGIC);
8  end Negative_D_Latch;
9
10 architecture Behavioral of Negative_D_Latch is
11     signal DATA : STD_LOGIC;
12 begin
13
14     DATA <= D when (EN = '0') else DATA;
15     Q <= DATA;
16
17 end Behavioral;

```

Figure 13: Negative D-Latch VHDL Code.

 


Figure 14: BDF file of the VHDL code generated from figure 13 into a symbol with inputs and outputs.



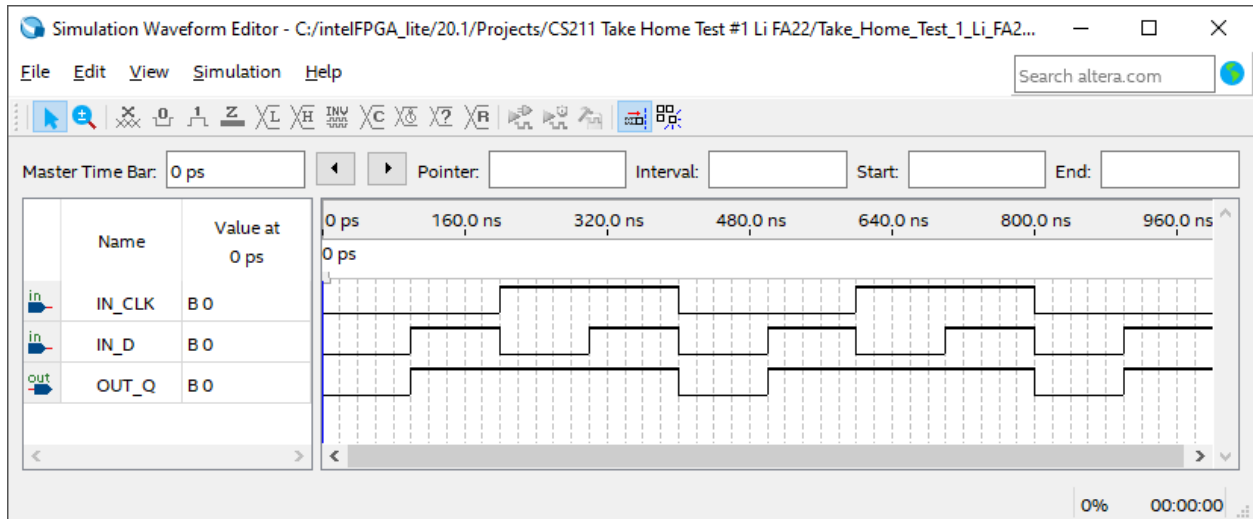


Figure 15: VWF output of the VHDL Code in Figure 13 generated as a symbol with input signals `IN_CLK` and `IN_D` and output signal `OUT_Q`.

```

1  -- Copyright (C) 2020 Intel Corporation. All rights reserved.
2  -- Your use of Intel Corporation's design tools, logic functions
3  -- and other software and tools, and any partner logic
4  -- functions, and any output files from any of the foregoing
5  -- (including device programming or simulation files), and any
6  -- associated documentation or information are expressly subject
7  -- to the terms and conditions of the Intel Program License
8  -- Subscription Agreement, the Intel Quartus Prime License Agreement,
9  -- the Intel FPGA IP License Agreement, or other applicable license
10 -- agreement, including, without limitation, that your use is for
11 -- the sole purpose of programming logic devices manufactured by
12 -- Intel and sold by Intel or its authorized distributors. Please
13 -- refer to the applicable agreement for further details, at
14 -- https://fpgasoftware.intel.com/eula.
15
16 -- PROGRAM      "Quartus Prime"
17 -- VERSION      "Version 20.1.1 Build 720 11/11/2020 SJ Lite Edition"
18 -- CREATED      "Sun Nov 06 20:14:43 2022"
19
20 LIBRARY ieee;
21 USE ieee.std_logic_1164.all;
22
23 LIBRARY work;
24
25 ENTITY UpdatedPositiveDataLatchusingGatesVHDL IS
26     PORT
27     (
28         A0 : IN  STD_LOGIC;
29         A1 : IN  STD_LOGIC;
30         S  : IN  STD_LOGIC;
31         Y  : OUT STD_LOGIC
32     );
33 END UpdatedPositiveDataLatchusingGatesVHDL;
34
35 ARCHITECTURE bdf_type OF UpdatedPositiveDataLatchusingGatesVHDL IS
36
37     SIGNAL SYNTHESIZED_WIRE_0 : STD_LOGIC;
38     SIGNAL SYNTHESIZED_WIRE_1 : STD_LOGIC;
39     SIGNAL SYNTHESIZED_WIRE_2 : STD_LOGIC;
40     SIGNAL SYNTHESIZED_WIRE_3 : STD_LOGIC;
41
42
43 BEGIN
44     Y <= SYNTHESIZED_WIRE_0;
45
46
47     SYNTHESIZED_WIRE_3 <= SYNTHESIZED_WIRE_0 AND SYNTHESIZED_WIRE_1;
48
49     SYNTHESIZED_WIRE_2 <= A1 AND S;
50
51     SYNTHESIZED_WIRE_1 <= NOT(S);
52
53     SYNTHESIZED_WIRE_0 <= SYNTHESIZED_WIRE_2 OR SYNTHESIZED_WIRE_3;
54
55
56
57
58
59
60
61 END bdf_type;

```

Figure 16: Positive D-Latch digital VHDL Code generated using Quartus HDL Design.

```

1  -- Copyright (C) 2020 Intel Corporation. All rights reserved.
2  -- Your use of Intel Corporation's design tools, logic functions
3  -- and other software and tools, and any partner logic
4  -- functions, and any output files from any of the foregoing
5  -- (including device programming or simulation files), and any
6  -- associated documentation or information are expressly subject
7  -- to the terms and conditions of the Intel Program License
8  -- Subscription Agreement, the Intel Quartus Prime License Agreement,
9  -- the Intel FPGA IP License Agreement, or other applicable license
10 -- agreement, including, without limitation, that your use is for
11 -- the sole purpose of programming logic devices manufactured by
12 -- Intel and sold by Intel or its authorized distributors. Please
13 -- refer to the applicable agreement for further details, at
14 -- https://fpgasoftware.intel.com/eula.
15
16 -- PROGRAM      "Quartus Prime"
17 -- VERSION      "Version 20.1.1 Build 720 11/11/2020 SJ Lite Edition"
18 -- CREATED      "Sun Nov 06 20:16:18 2022"
19
20 LIBRARY ieee;
21 USE ieee.std_logic_1164.all;
22
23 LIBRARY work;
24
25 ENTITY UpdatedNegativeDataLatchUsingGatesVHDL IS
26     PORT
27     (
28         A0 : IN  STD_LOGIC;
29         A1 : IN  STD_LOGIC;
30         S  : IN  STD_LOGIC;
31         Y  : OUT STD_LOGIC
32     );
33 END UpdatedNegativeDataLatchUsingGatesVHDL;
34
35 ARCHITECTURE bdf_type OF UpdatedNegativeDataLatchUsingGatesVHDL IS
36
37     SIGNAL SYNTHESIZED_WIRE_6 : STD_LOGIC;
38     SIGNAL SYNTHESIZED_WIRE_1 : STD_LOGIC;
39     SIGNAL SYNTHESIZED_WIRE_2 : STD_LOGIC;
40     SIGNAL SYNTHESIZED_WIRE_4 : STD_LOGIC;
41     SIGNAL SYNTHESIZED_WIRE_5 : STD_LOGIC;
42
43
44 BEGIN
45     Y <= SYNTHESIZED_WIRE_1;
46
47
48
49     SYNTHESIZED_WIRE_4 <= A1 AND SYNTHESIZED_WIRE_6;
50
51
52     SYNTHESIZED_WIRE_5 <= SYNTHESIZED_WIRE_1 AND SYNTHESIZED_WIRE_2;
53
54
55     SYNTHESIZED_WIRE_6 <= NOT(S);
56
57
58
59     SYNTHESIZED_WIRE_2 <= NOT(SYNTHESIZED_WIRE_6);
60
61
62
63     SYNTHESIZED_WIRE_1 <= SYNTHESIZED_WIRE_4 OR SYNTHESIZED_WIRE_5;
64
65
66 END bdf_type;

```

Figure 17: Negative D-Latch digital VHDL Code generated using Quartus HDL Design.

## ***Conclusions:***

In this report, I learned about one of the many applications of the 2:1 Multiplexer. One of them being a D-Latch. The equation of a 2:1 Mux is  $Y = SA * 0 + S' * A1$  and we can rewrite that to fit the purpose of D-Latch because the logic of the D-Latch can be interpreted as if Clock is high, then Q follows D else Q follows Q which can be written as  $\text{Clock} * D + \text{Clock}' * Q$ . I also learned about the difference between positive and Negative D-Latches. Positive D-Latch refers to when the clock pulse transitions from a low to high (0 to 1) and is called a rising edge. Negative D-Latch refers to when the clock pulse transitions from high to low (1 to 0) and is called a falling edge. Through this report, I also developed a better understanding of D-Latches, Multiplexers, and writing VHDL code.