

City College of New York

## Take Home Test # 2

Zi Xuan Li

CSC 211 Fall 2022

Professor Izidor Gertner

November 13<sup>th</sup>, 2022

## Objective:

The objective of this lab report is to build, simulate, and verify the correctness of both the Rising Edge D-Flipflops and Falling Edge D-Flipflops. This report will compose of Rising and Falling Edge D-Flipflops built using AND, OR, and NOT gates built in a template of 2:1 Multiplexers, as well as Rising and Falling Edge D-Flipflops built using 2:1 Multiplexers as symbols, and lastly Rising and Falling Edge D-Flipflops built using the DFF found in the library of Quartus components. Alongside the D-Flipflops, the report will also demonstrate VHDL code for the Rising and Falling D-Flipflop as well as simulation of the code using the Quartus “Create Symbol file from current VHDL File” function. Finally, the report will conclude with a simulation comparison of a level sensitive D-Latch, Rising Edge D-Flipflop, and a Falling Edge D-Flipflop.



## Functionality, Specifications, and Simulation:



To verify the correctness of these digital circuits, we must first understand what a D-FF is and how a Rising Edge and Falling Edge D-FF works.

The D-FF is a flip flop that contains two inputs. Those inputs are the data (D) input and the clock (CLK) input. The D-FF is used to delay the change of state of its output signal (Q) until the next rising edge of the clock signal occurs. This means that the output of the flipflop changes with the transition of the clock pulse, either from low to high or high to low in the case of the falling edge D-FF.

The Rising Edge D-FF is a circuit that changes its output (Q) in accordance with the input (D) during the positive transition of the clock (CLK) pulse of the flipflop. This implies that the D-FF is a flip-flop in which the output can only change with the edge of the clock pulse, regardless of the change in the input. In other words, unless the Rising Edge D-FF’s clock input is changing from 0 to 1, the flipflop stays in a hold state.

The Falling Edge D-FF is a circuit that changes its output (Q) in accordance with the input (D) during the negative transition of the clock (CLK) pulse of the flipflop. This implies that the D-FF is a flip-flop in which the output can only change with the edge of the clock pulse, regardless of the change in the input. But unlike the Rising Edge D-FF, unless the Falling Edge D-FF’s clock input is changing from 1 to 0, the flipflop stays in a hold state.

| Rising Edge D-Flipflop  |   |          |
|---|---|----------|
| CLK   | D | Q(t)     |
| 0   | 0 | $Q(t-1)$ |
| 0   | 1 | $Q(t-1)$ |
|  | 0 | 0        |
|  | 1 | 1        |
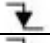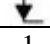
| Falling Edge D-Flipflop   |   |          |
|---|---|----------|
| CLK   | D | Q(t)     |
|  | 0 | 0        |
|  | 1 | 1        |
| 1   | 0 | $Q(t-1)$ |
| 1   | 1 | $Q(t-1)$ |

**Part 1: (Design and build in Quartus Rising Edge D-FF using 2:1 MUX using gates from the first lab)**

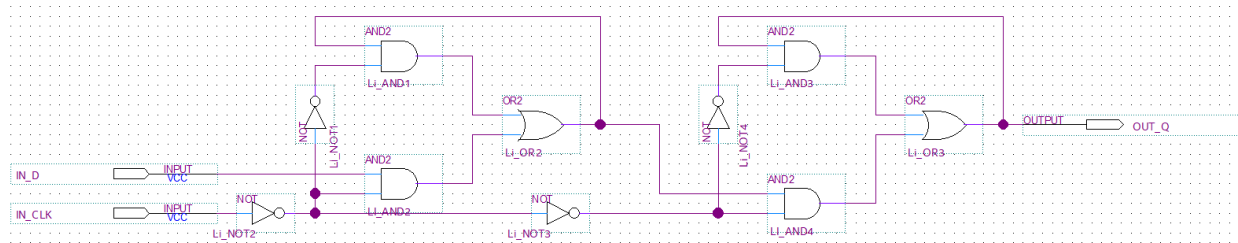


Figure 1: Rising Edge D-FF built using the 2:1 Mux as a template with AND, OR, and NOT gates.

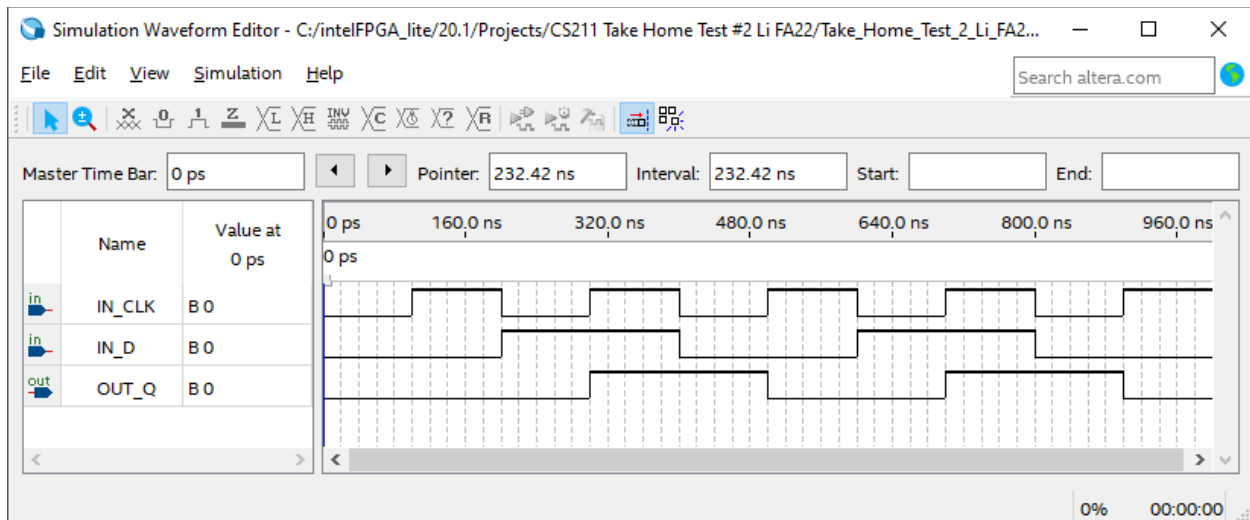


Figure 2: University VWF output for the Rising Edge D-FF built in figure 1 with input signals IN\_CLK, IN\_D and output signal OUT\_Q. The duty cycles of the signals remain at 50%, however the period of IN\_CLK is 200ns and IN\_D is 400ns.

| Rising Edge D-Flipflop |   |          |
|------------------------|---|----------|
| CLK                    | D | Q(t)     |
| 0                      | 0 | $Q(t-1)$ |
| 0                      | 1 | $Q(t-1)$ |
|                        | 0 | 0        |
|                        | 1 | 1        |

To verify the correctness of the Rising Edge D-FF built using 2:1 Mux as a template with AND, OR, and NOT gates. We can compare the instances where the input IN\_CLK is transitioning from (0 to 1) i.e., when a rising edge occurs in the CLK signal to the Rising Edge D-FF truth table. In this case, the first rising edge occurs between 0 ns and 160ns where IN\_D is low, we can see that OUT\_Q is also low. The second rising edge occurs between 160ns and 320ns where IN\_D is high, and we can see that OUT\_Q is also high. Looking at the timestamps between those instances, we can see that OUT\_Q is holding onto the previous value of Q unless IN\_D changes during the CLK's rising edge. With that information, we can map the rest of the inputs and outputs and conclude that the waveform simulation is correct.

## Part 2: (Design and build in Quartus Falling Edge D-FF using 2:1 MUX using gates from the first lab)

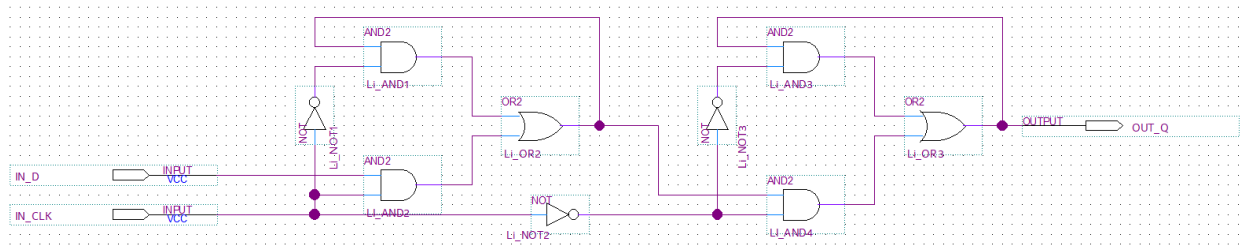


Figure 3: Falling Edge D-FF built using the 2:1 Mux as a template with AND, OR, and NOT gates.

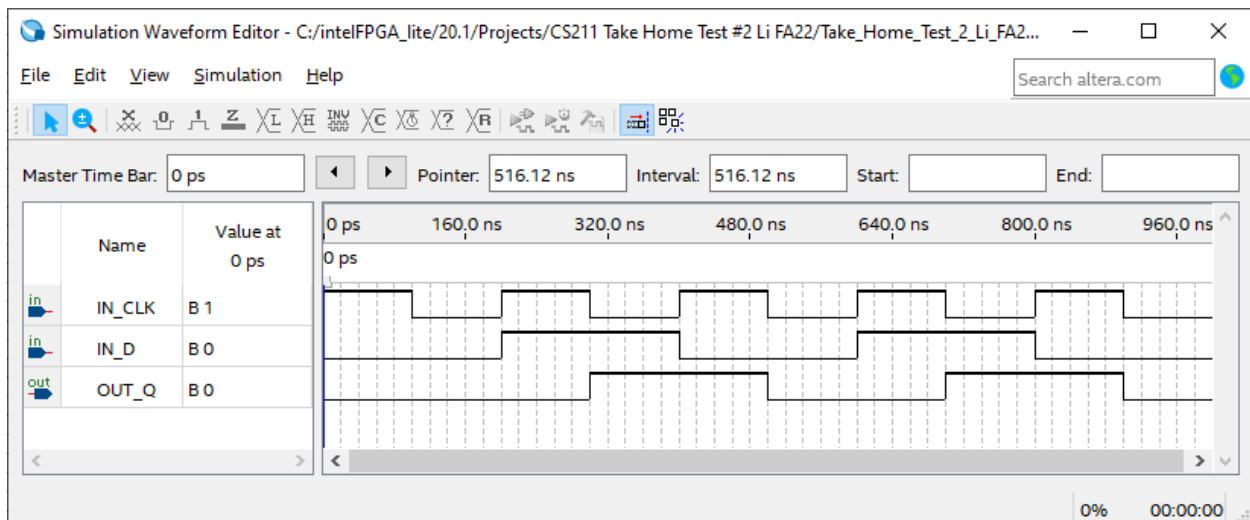


Figure 4: University VWF output for the Falling Edge D-FF built in figure 3 with input signals  $IN\_CLK$ ,  $IN\_D$  and output signal  $OUT\_Q$ . The duty cycle remains at 50%, however the period of  $IN\_CLK$  is 200ns and inverted and  $IN\_D$  is 400ns.

| Falling Edge D-Flipflop |   |          |
|-------------------------|---|----------|
| CLK                     | D | Q(t)     |
|                         | 0 | 0        |
|                         | 1 | 1        |
| 1                       | 0 | $Q(t-1)$ |
| 1                       | 1 | $Q(t-1)$ |

To verify the correctness of the Falling Edge D-FF built using 2:1 Mux as a template with AND, OR, and NOT gates. We can compare the instances where the input  $IN\_CLK$  is transitioning from (1 to 0) i.e., when a falling edge occurs in the CLK signal to the Falling Edge D-FF truth table. In this case, the first falling edge occurs between 0 ns and 160ns where  $IN\_D$  is low, we can see that  $OUT\_Q$  is also low. The second falling edge occurs between 160ns and 320ns where  $IN\_D$  is high, and we can see that  $OUT\_Q$  is also high. Looking at the timestamps between those instances, we can see that  $OUT\_Q$  is holding onto the previous value of Q unless  $IN\_D$  changes during the CLK's falling edge. With that information, we can map the rest of the inputs and outputs and conclude that the waveform simulation is correct.

**Part 3: (Design and build in Quartus Rising Edge D-FF using 2:1 MUX using Quartus component symbol)**

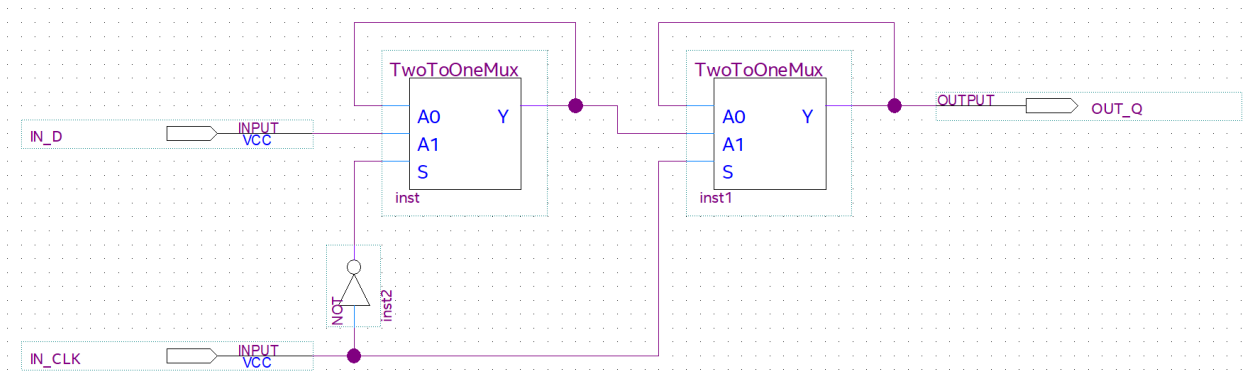


Figure 5: Rising Edge D-FF built using the 2:1 Mux symbol as a component.

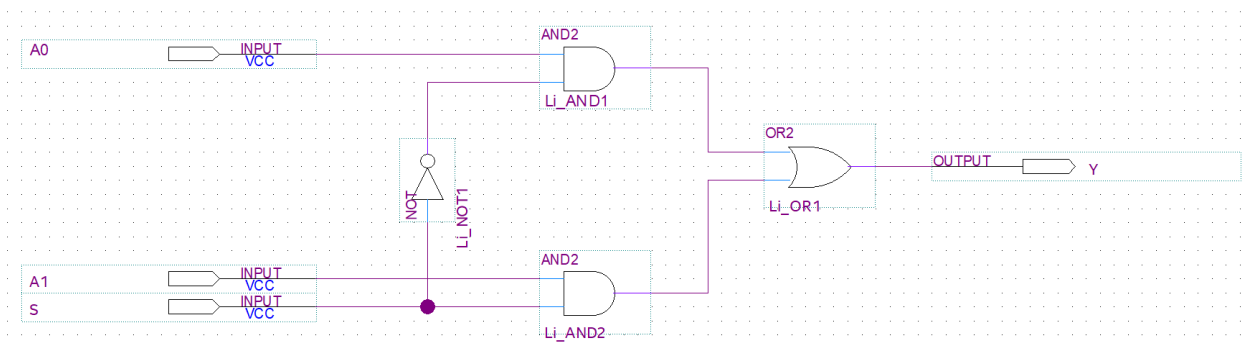


Figure 6: Circuit diagram of the 2:1 Mux symbol used in the Rising Edge D-FF in figure 5.

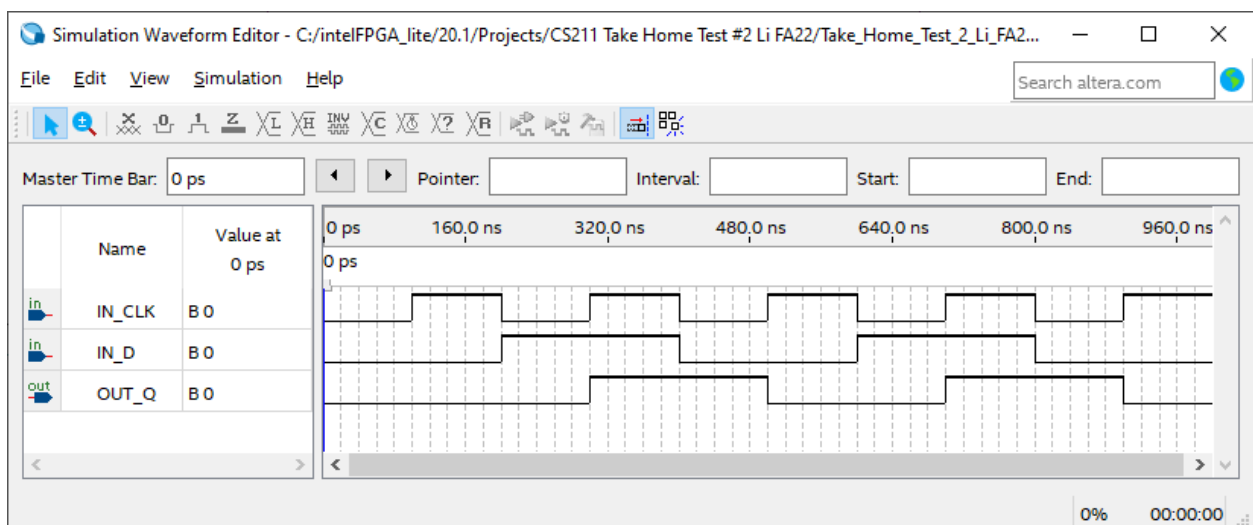


Figure 7: University VWF output for the Rising Edge D-FF built in figure 5 with input signals IN\_CLK, IN\_D and output signal OUT\_Q. The duty cycles of the signals remain at 50%, however the period of IN\_CLK is 200ns and IN\_D is 400ns.

| Rising Edge D-Flipflop  |   |          |
|---|---|----------|
| CLK   | D | Q(t)     |
| 0   | 0 | $Q(t-1)$ |
| 0   | 1 | $Q(t-1)$ |
|  | 0 | 0        |
|  | 1 | 1        |

To verify the correctness of the Rising Edge D-FF built using 2:1 Mux symbol as a component. We can compare the instances where the input IN\_CLK is transitioning from (0 to 1) i.e., when a rising edge occurs in the CLK signal to the Rising Edge D-FF truth table. In this case, the first rising edge occurs between 0 ns and 160ns where IN\_D is low, we can see that OUT\_Q is also low. The second rising edge occurs between 160ns and 320ns where IN\_D is high, and we can see that OUT\_Q is also high. Looking at the timestamps between those instances, we can see that OUT\_Q is holding onto the previous value of Q unless IN\_D changes during the CLK's rising edge. With that information, we can map the rest of the inputs and outputs and conclude that the waveform simulation is correct.

#### Part 4: (Design and build in Quartus Falling Edge D-FF using 2:1 MUX using Quartus component symbol)

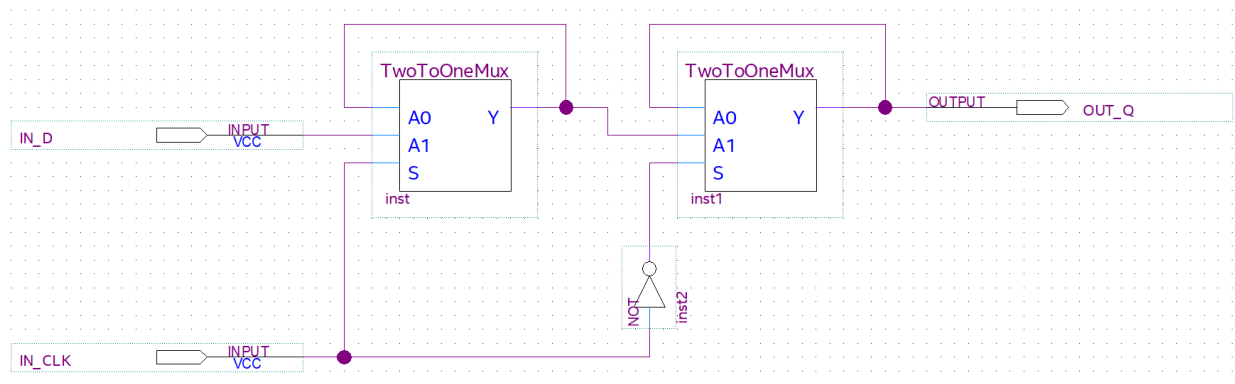


Figure 8: Falling Edge D-FF built using the 2:1 Mux symbol as a component.

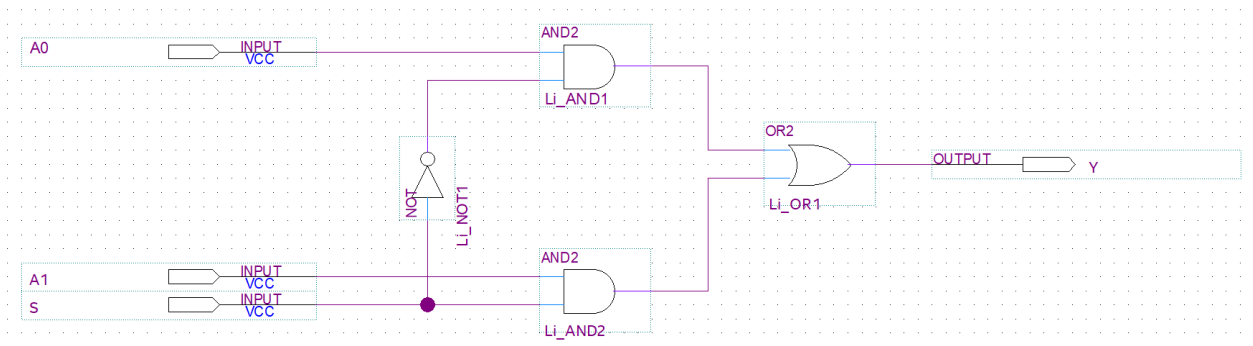


Figure 9: Circuit diagram of the 2:1 Mux symbol used in the Falling Edge D-FF in figure 8.

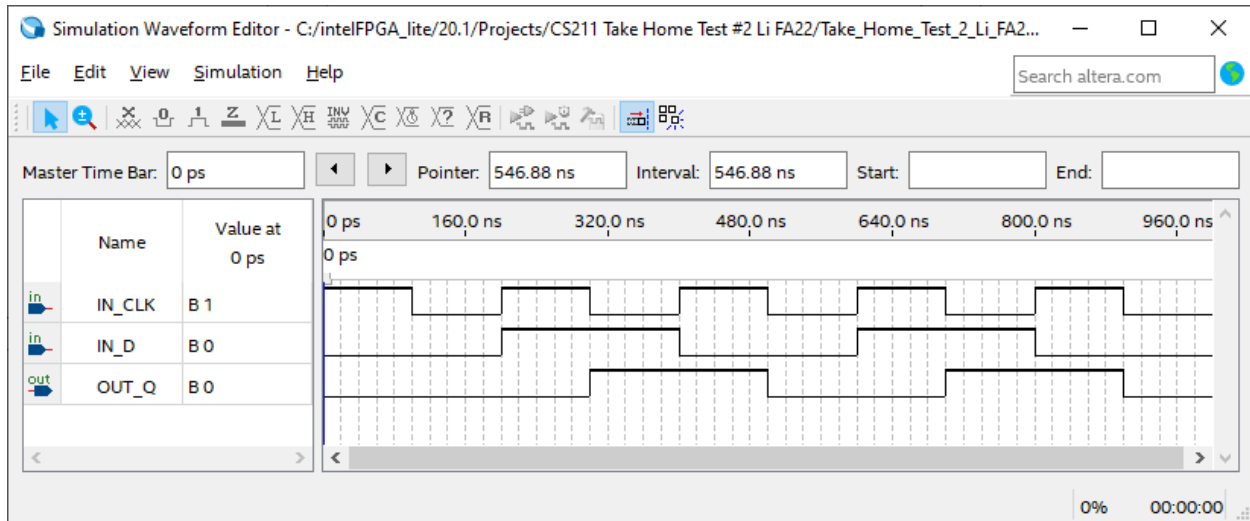


Figure 10: University VWF output for the Falling Edge D-FF built in figure 8 with input signals  $IN\_CLK$ ,  $IN\_D$  and output signal  $OUT\_Q$ . The duty cycle remains at 50%, however the period of  $IN\_CLK$  is 200ns and inverted and  $IN\_D$  is 400ns.

| Falling Edge D-Flipflop |   |          |
|-------------------------|---|----------|
| CLK                     | D | Q(t)     |
| $\downarrow$            | 0 | 0        |
| $\downarrow$            | 1 | 1        |
| 1                       | 0 | $Q(t-1)$ |
| 1                       | 1 | $Q(t-1)$ |

To verify the correctness of the Falling Edge D-FF FF built using 2:1 Mux symbol as a component. We can compare the instances where the input  $IN\_CLK$  is transitioning from (1 to 0) i.e., when a falling edge occurs in the CLK signal to the Falling Edge D-FF truth table. In this case, the first falling edge occurs between 0 ns and 160ns where  $IN\_D$  is low, we can see that  $OUT\_Q$  is also low. The second falling edge occurs between 160ns and 320ns where  $IN\_D$  is high, and we can see that  $OUT\_Q$  is also high. Looking at the timestamps between those instances, we can see that  $OUT\_Q$  is holding onto the previous value of Q unless  $IN\_D$  changes during the CLK's falling edge. With that information, we can map the rest of the inputs and outputs and conclude that the waveform simulation is correct.

**Part 5: (Write YOUR OWN VHDL code for Rising Edge D-FF, Falling Edge D-FF. Create a separate Quartus project for each)**

```

1  Library IEEE;
2  USE IEEE.Std_logic_1164.all;
3
4  entity RisingEdgeDFlipFlop is
5  port
6  (
7      Q : out std_logic;
8      Clk :in std_logic;
9      D :in  std_logic
10 );
11
12 end RisingEdgeDFlipFlop;
13
14 architecture Behavioral of RisingEdgeDFlipFlop is
15 begin
16     process(Clk)
17     begin
18
19         if(rising_edge(Clk)) then
20             Q <= D;
21         end if;
22     end process;
23 end Behavioral;

```

Figure 11: VHDL code of a Rising Edge D-FF.

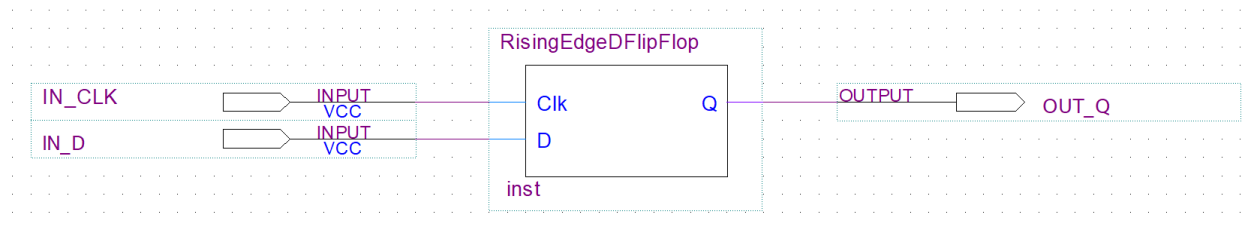


Figure 12: Circuit Diagram created using the symbol generated from the VHDL code in figure 11.

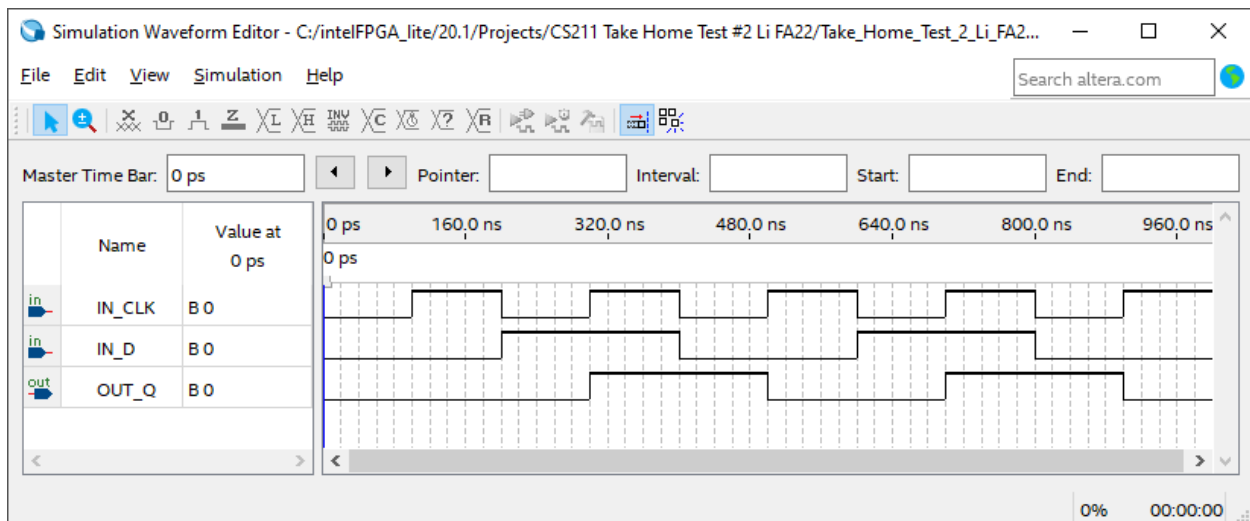


Figure 13: University VWF output for the Rising Edge D-FF built in figure 12 with input signals IN\_CLK, IN\_D and output signal OUT\_Q. The duty cycles of the signals remain at 50%, however the period of IN\_CLK is 200ns and IN\_D is 400ns.



| Rising Edge D-Flipflop  |   |          |
|---|---|----------|
| CLK   | D | Q(t)     |
| 0   | 0 | $Q(t-1)$ |
| 0   | 1 | $Q(t-1)$ |
|  | 0 | 0        |
|  | 1 | 1        |

To verify the correctness of the Rising Edge D-FF FF built using a symbol generated from VHDL code. We can compare the instances where the input IN\_CLK is transitioning from (0 to 1) i.e., when a rising edge occurs in the CLK signal to the Rising Edge D-FF truth table. In this case, the first rising edge occurs between 0 ns and 160ns where IN\_D is low, we can see that OUT\_Q is also low. The second rising edge occurs between 160ns and 320ns where IN\_D is high, and we can see that OUT\_Q is also high. Looking at the timestamps between those instances, we can see that OUT\_Q is holding onto the previous value of Q unless IN\_D changes during the CLK's rising edge. With that information, we can map the rest of the inputs and outputs and conclude that the waveform simulation is correct.

```

1  Library IEEE;
2  USE IEEE.Std_logic_1164.all;
3
4  entity FallingEdgeDFlipFlop is
5  port
6  (
7      Q : out std_logic;
8      Clk :in std_logic;
9      D :in std_logic
10 );
11
12 end FallingEdgeDFlipFlop;
13
14 architecture Behavioral of FallingEdgeDFlipFlop is
15 begin
16     process(c1k)
17     begin
18
19         if(falling_edge(c1k)) then
20             Q <= D;
21         end if;
22     end process;
23 end Behavioral;

```

Figure 14: VHDL code of a Falling Edge D-FF.

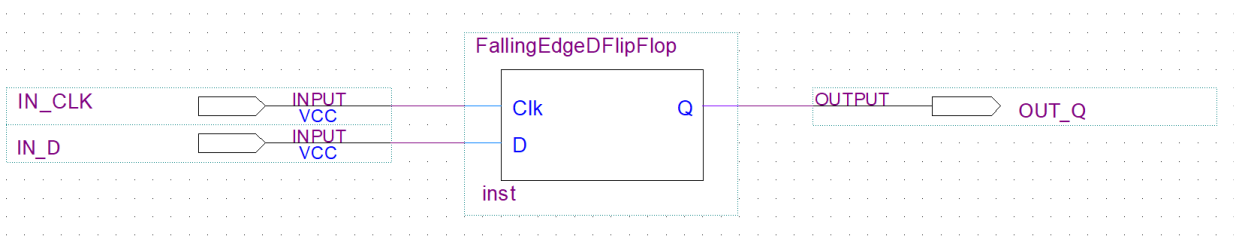


Figure 15: Circuit Diagram created using the symbol generated from the VHDL code in figure 14.

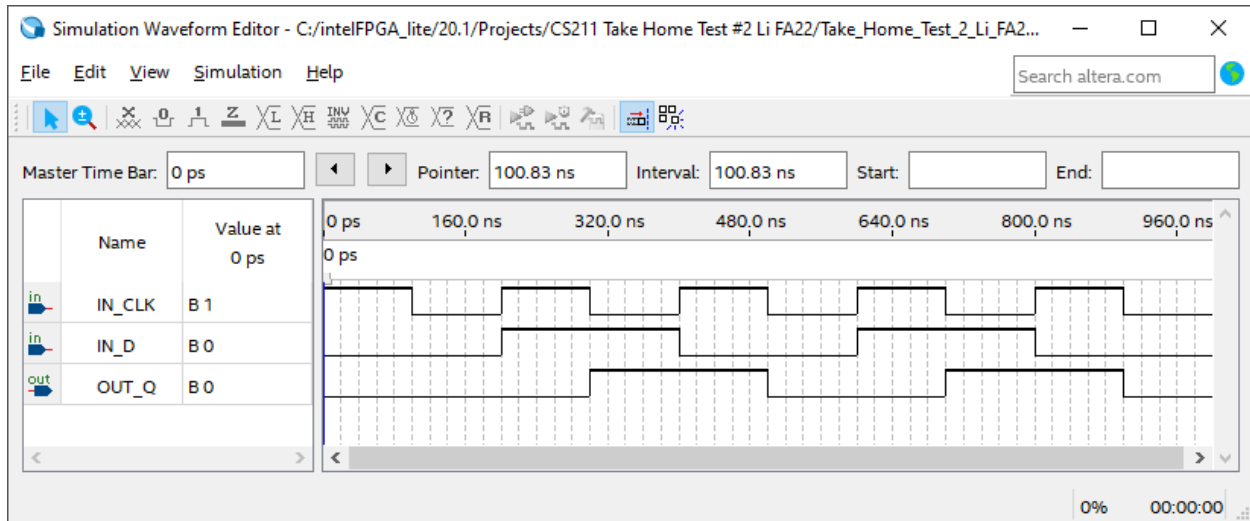


Figure 16: University VWF output for the Falling Edge D-FF built in figure 15 with input signals IN\_CLK, IN\_D and output signal OUT\_Q. The duty cycle remains at 50%, however the period of IN\_CLK is 200ns and inverted and IN\_D is 400ns.

| Falling Edge D-Flipflop |   |          |
|-------------------------|---|----------|
| CLK                     | D | Q(t)     |
| $\downarrow$            | 0 | 0        |
| $\downarrow$            | 1 | 1        |
| 1                       | 0 | $Q(t-1)$ |
| 1                       | 1 | $Q(t-1)$ |

To verify the correctness of the Falling Edge D-FF built using a symbol generated from VHDL code. We can compare the instances where the input IN\_CLK is transitioning from (1 to 0) i.e., when a falling edge occurs in the CLK signal to the Falling Edge D-FF truth table. In this case, the first falling edge occurs between 0 ns and 160ns where IN\_D is low, we can see that OUT\_Q is also low. The second falling edge occurs between 160ns and 320ns where IN\_D is high, and we can see that OUT\_Q is also high. Looking at the timestamps between those instances, we can see that OUT\_Q is holding onto the previous value of Q unless IN\_D changes during the CLK's falling edge. With that information, we can map the rest of the inputs and outputs and conclude that the waveform simulation is correct.

## Part 6: (Design and build in Quartus Rising Edge D-FF using Quartus component symbol for D-FlipFlop)

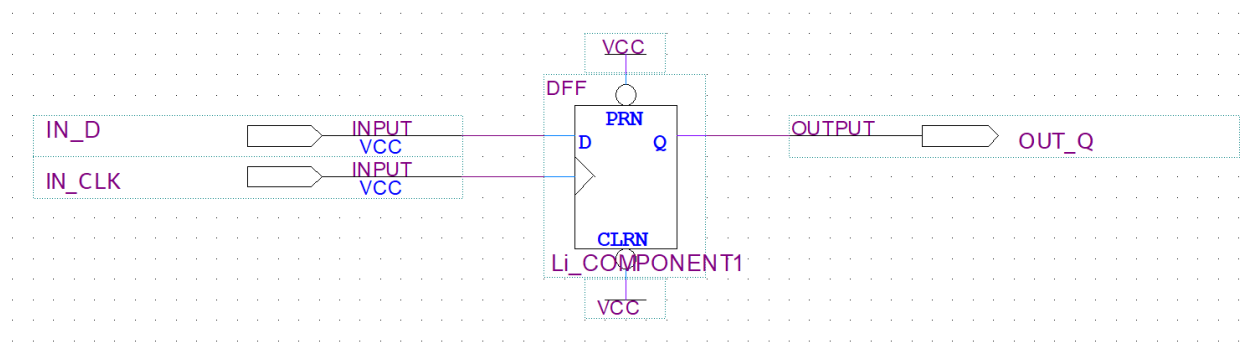


Figure 17: Rising Edge D-FF built using the DFF found in Quartus's library of components.

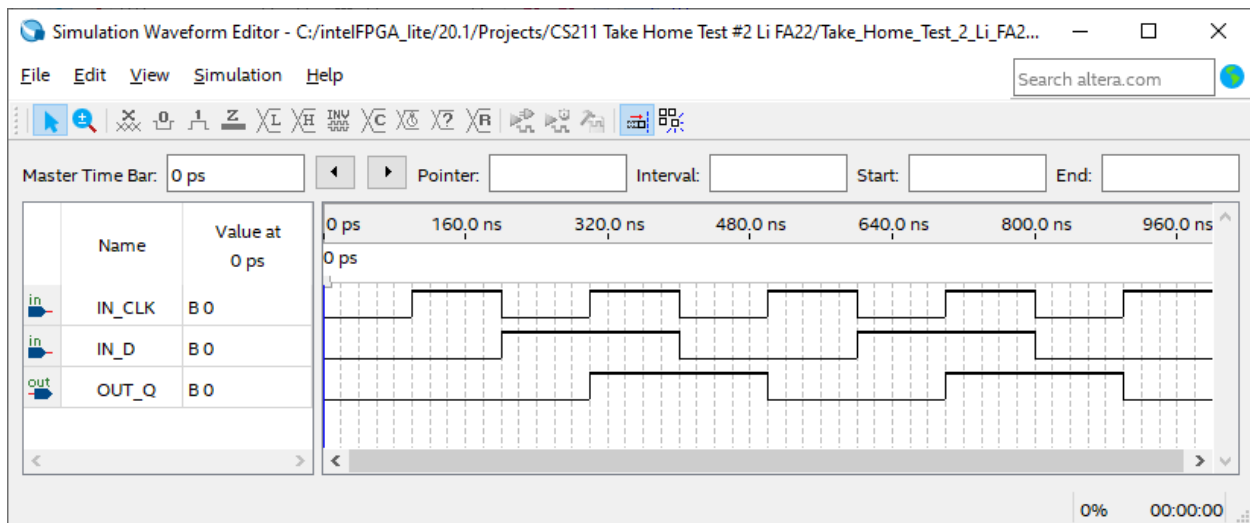


Figure 18: University VWF output for the Rising Edge D-FF built in figure 17 with input signals *IN\_CLK*, *IN\_D* and output signal *OUT\_Q*. The duty cycles of the signals remain at 50%, however the period of *IN\_CLK* is 200ns and *IN\_D* is 400ns.

## Part 7: (Design and build in Quartus Falling Edge D-FF using Quartus component symbol for D-FlipFlop)

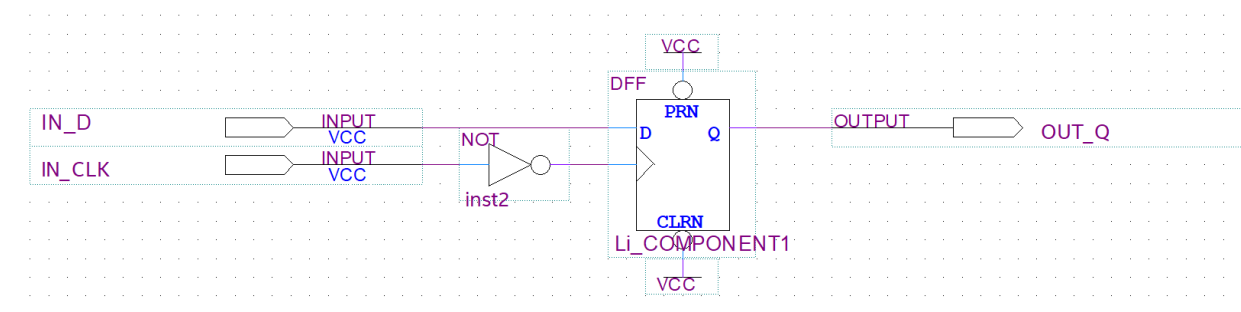


Figure 19: Falling Edge D-FF built using the DFF found in Quartus's library of components.

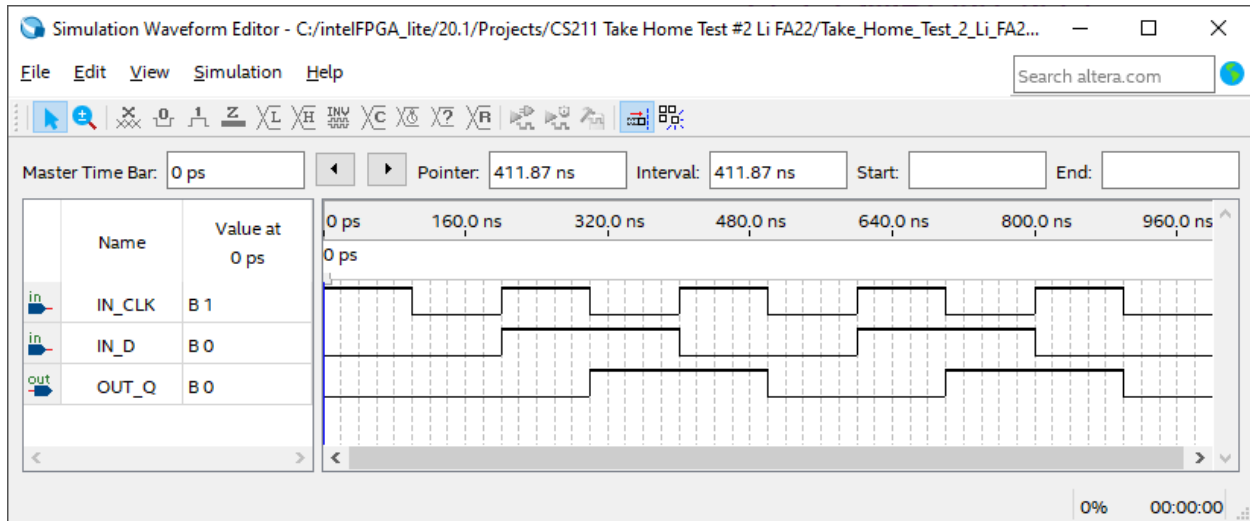


Figure 20: University VWF output for the Falling Edge D-FF built in figure 19 with input signals IN\_CLK, IN\_D and output signal OUT\_Q. The duty cycle remains at 50%, however the period of IN\_CLK is 200ns and inverted and IN\_D is 400ns.

#### Part 8: (Compare in simulation case 5 with cases 7 and 8.)

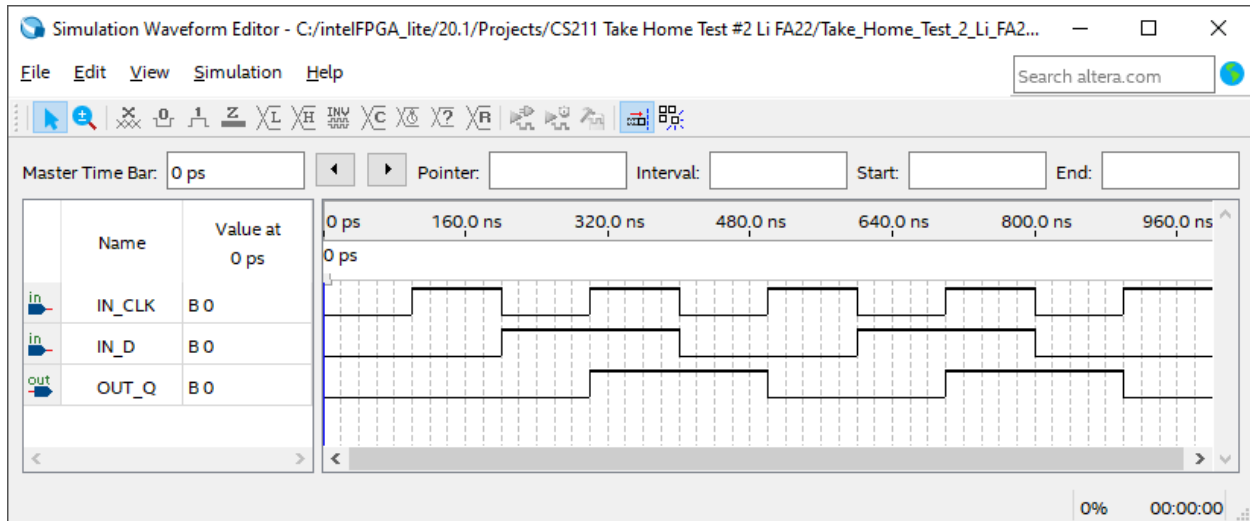


Figure 21: University VWF output for the Rising Edge D-FF built in figure 12 with input signals IN\_CLK, IN\_D and output signal OUT\_Q. The duty cycles of the signals remain at 50%, however the period of IN\_CLK is 200ns and IN\_D is 400ns.

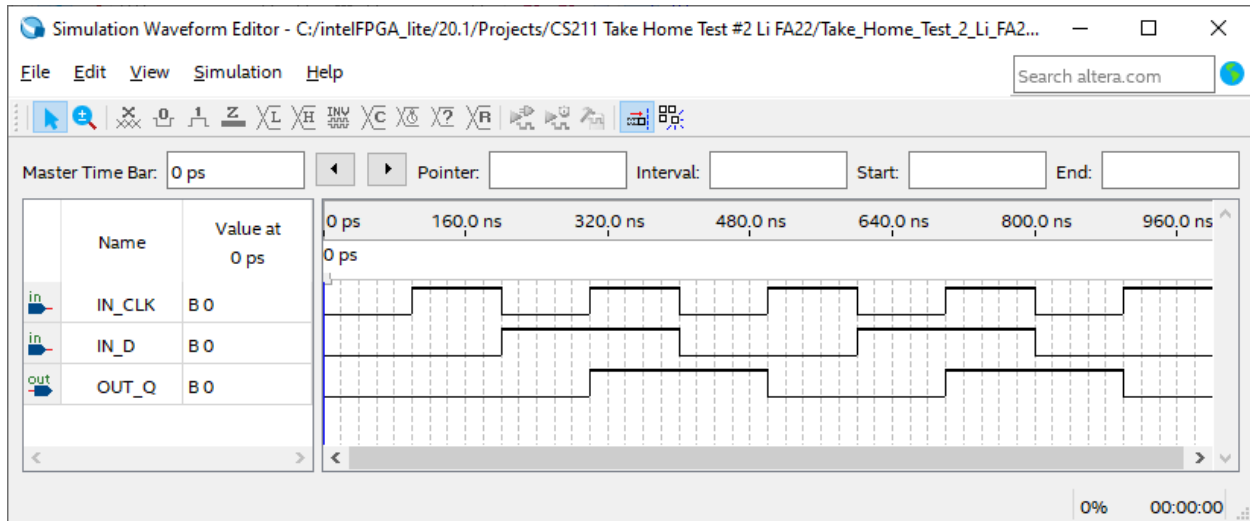


Figure 22: University VWF output for the Rising Edge D-FF built in figure 17 with input signals IN\_CLK, IN\_D and output signal OUT\_Q. The duty cycles of the signals remain at 50%, however the period of IN\_CLK is 200ns and IN\_D is 400ns.

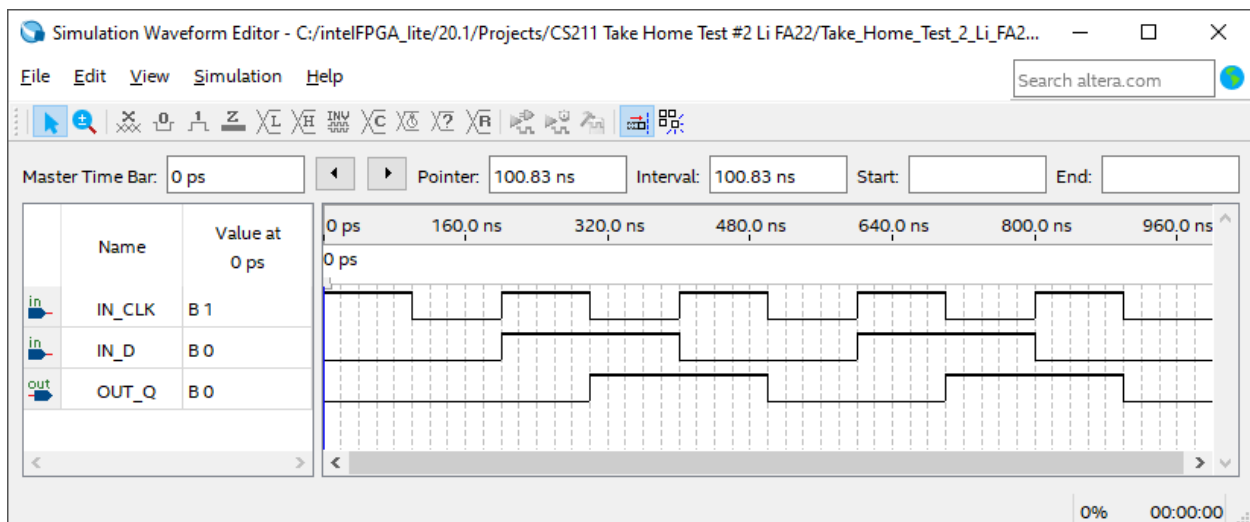


Figure 23: University VWF output for the Falling Edge D-FF built in figure 15 with input signals IN\_CLK, IN\_D and output signal OUT\_Q. The duty cycle remains at 50%, however the period of IN\_CLK is 200ns and inverted and IN\_D is 400ns.

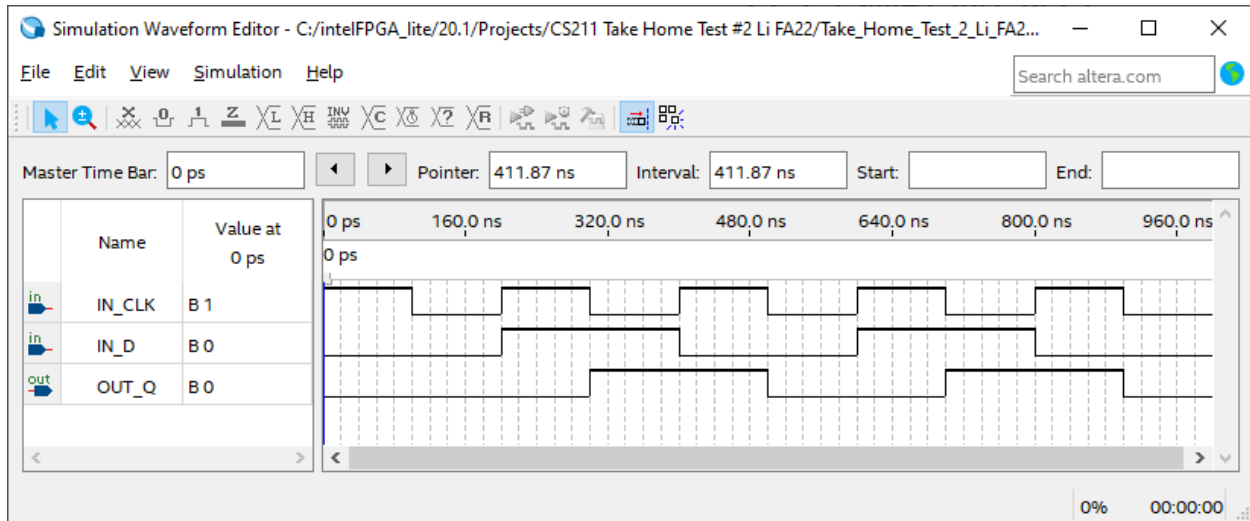


Figure 24: University VWF output for the Falling Edge D-FF built in figure 19 with input signals IN\_CLK, IN\_D and output signal OUT\_Q. The duty cycle remains at 50%, however the period of IN\_CLK is 200ns and inverted and IN\_D is 400ns.

Comparing the waveforms from Part 5.a to Part 7 and Part 5.b to Part 8, we can see that there are no differences between the output OUT\_Q of the digital circuits when their inputs IN\_CLK and IN\_D are the same. With the knowledge of the fact that Part 7 and 8 are built using Quartus library components, we know that the waveform simulation are correct. Comparing and constrasting them, we can see that they have no differences at all, therefore the waveforms built using VHDL code are correct.

### Part 9: (Create in simulation timing diagram shown on the next page for all devices

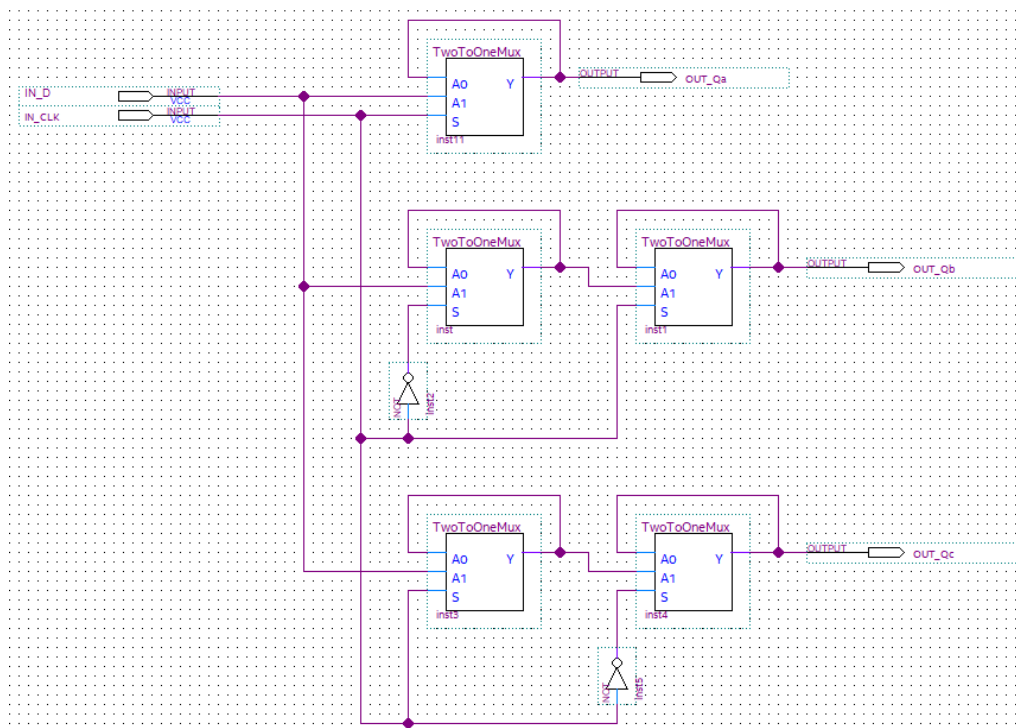


Figure 25: Circuit diagram of D-Latch, Rising Edge D-FF, Falling Edge D-FF with inputs IN\_D, IN\_CLK and outputs OUT\_Qa, OUT\_Qb, and OUT\_Qc representing D-Latch, Rising Edge D-FF, and Falling Edge D-FF respectively.

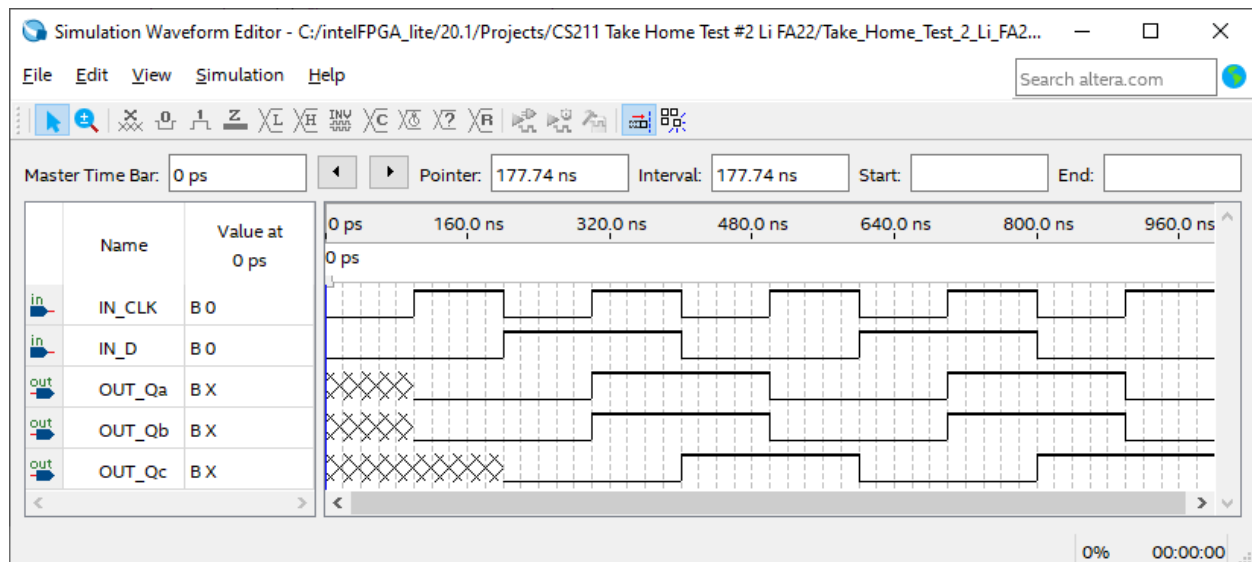


Figure 26: University VWF output for the circuit built in figure 21 with input signals IN\_CLK, IN\_D and output signal OUT\_Qa, OUT\_Qb, and OUT\_Qc representing D-Latch, Rising Edge D-FF, and Falling Edge D-FF respectively. The duty cycle of the inputs remains at 50%, however the period of IN\_CLK is 200ns and IN\_D is 400ns.

| D Latch |   |          |
|---------|---|----------|
| CLK     | D | Q(t)     |
| 0       | 0 | $Q(t-1)$ |
| 0       | 1 | $Q(t-1)$ |
| 1       | 0 | 0        |
| 1       | 1 | 1        |

| Rising Edge D-Flipflop |   |          |
|------------------------|---|----------|
| CLK                    | D | Q(t)     |
| 0                      | 0 | $Q(t-1)$ |
| 0                      | 1 | $Q(t-1)$ |
|                        | 0 | 0        |
|                        | 1 | 1        |

| Falling Edge D-Flipflop |   |          |
|-------------------------|---|----------|
| CLK                     | D | Q(t)     |
|                         | 0 | 0        |
|                         | 1 | 1        |
| 1                       | 0 | $Q(t-1)$ |
| 1                       | 1 | $Q(t-1)$ |

To verify the correctness of the 3 different waveform simulations we can compare OUT\_Qa to the truth table of the D-Latch, OUT\_Qb to the truth table of the rising edge D-Flipflop, and OUT\_Qc to the truth table of the falling edge D-Flipflop. For the waveform of OUT\_Qa, we can see when IN\_CLK is high and IN\_D is low that OUT\_Qa is also low. We can also see for OUT\_Qa when IN\_CLK is high and IN\_D is high that OUT\_Qa is also high. Otherwise, OUT\_Qa is always holding onto the previous output of OUT\_Qa until IN\_CLK is high and IN\_D changes state. For the waveform of OUT\_Qb, we can see when IN\_CLK changes from 0 to 1 and IN\_D is 0 that OUT\_Qb is also 0. We can also see for OUT\_Qb when IN\_CLK changes from 0 to 1 and IN\_D is 1 that OUT\_Qb is also 1. Otherwise, OUT\_Qb is always holding onto the previous output of OUT\_Qb unless IN\_CLK transitions from 0 to 1 and IN\_D changes state. For the waveform of OUT\_Qc, we can see when IN\_CLK changes from 1 to 0 and IN\_D is 0 that OUT\_Qc is also 0. We can also see for OUT\_Qc when IN\_CLK changes from 1 to 0 and IN\_D is 1 that OUT\_Qc is also 1. Otherwise, OUT\_Qc is always holding onto the previous output of OUT\_Qc unless IN\_CLK transitions from 1 to 0 and IN\_D changes state. With all this information, we can compare this to their respective truth tables and determine that the waveform simulations are correct.

### ***Conclusions:***

In this report, I learned about another application of the 2:1 Multiplexer. Previously, I learned that the 2:1 Multiplexer can be wired to act like a D-Latch. This time, I learned that two 2:1 Multiplexers can be wired in such a way to function like a D-Flipflop. By generating a latch using a mux and using back-to-back latches at different clock edges, two 2:1 Multiplexers can function like a flip flop. I also learned about Rising Edge as well as Falling edge and their applications in digital electronic circuits. Rising Edge refers to when the clock pulse transitions from low to high (0 to 1) and falling edge refers to when the clock pulse transitions from high to low (1 to 0).